

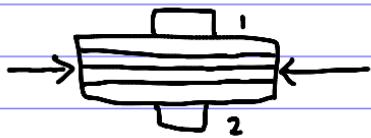



1)

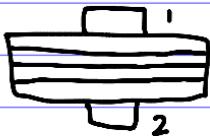

Axial

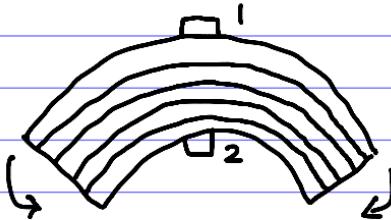

Bending

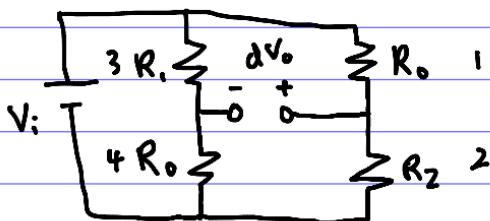

$$S_1 = S^a + S^b + S^t$$

$$S_2 = S^a - S^b + S^t$$

$$\frac{dv_o}{v_i} = \frac{1}{4} G \left( \frac{dR_2}{R_2} - \frac{dR_o}{R_o} + \frac{dR_1}{R_1} - \frac{dR_o}{R_o} \right)$$



$$= \frac{1}{4} G (S_2 + S_1)$$

$$= \frac{1}{4} G (S^a - S^b + S^t + S^a + S^b + S^t)$$

$$= \frac{1}{4} G (2S^a + 2S^t)$$

$$= \frac{1}{2} G (S^a + S^t)$$

2)

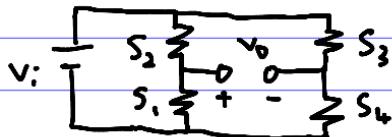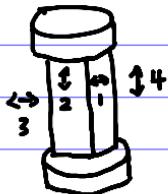

$$S_2 = S_4 = S^a + S^T$$

$$S_1 = S_3 = -S^a + S^T$$

$$= -\gamma S^a + S^T$$

$$\frac{V_o}{V_i} = \frac{1}{4} G (S_1 - S_2 + S_3 - S_4)$$

$$= \frac{1}{4} G (-\gamma S^a + S^T - S^a + S^T - \gamma S^a + S^T - S^a - S^T)$$

$$= \frac{1}{4} G (-2\gamma S^a - 2S^a)$$

$$= -\frac{1}{2} G (1 + \gamma) S^a$$

$$= -\frac{1+\gamma}{2} G S^a$$

$$2 \times V_{in} = 2 \rightarrow V_o$$

$$V_{max} = ?$$

$$I_{max} = 30mA$$

Nominal resistance,  $R_o$

$$V_{max} = 2R_o I$$

$$= 2(100)(30 \times 10^{-3})$$

$$= 6V$$

$$V_{max} \leq 6V$$

$$V_{amp} = K_{amp} V_o$$

$$V_o = \frac{V_{amp}}{K_{amp}}$$

$$\frac{V_o}{V_{in}} = \frac{V_{amp}}{K_{amp} V_{in}} = -\frac{1+\gamma}{2} G S^a$$

$$\frac{V_{amp}}{K_{amp} V_{in}} = -\frac{1+\gamma}{2} G \left( \frac{-F_o}{AE} \right)$$


$$K_{amp}$$

$$K_{amp} = \frac{2 V_{amp} AE}{(1+\gamma) G F_o V_{in}}$$

$$= \frac{2(1)(1 \times 10^{-2})(210 \times 10^9)}{(1+0.29)(2 \cdot 1)(10^5)(6)}$$

$$= 2583.979328$$

$$\approx 2584$$

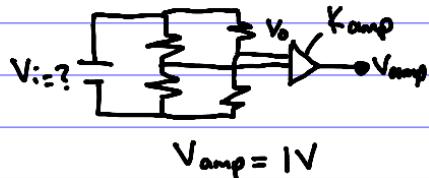

$$V_{amp} = 1V$$

$$3) \frac{dR}{R} = \left( \frac{d\rho}{\rho} \frac{1}{S} + 1 + 2\rho \right) S$$

$$R = \rho \left( \frac{L}{A} \right)$$

$$dR = d\rho \left( \frac{L}{A} \right) + dL \left( \frac{\rho}{A} \right) + \rho L d \left( \frac{1}{A} \right)$$

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} + \frac{dA}{A}$$

$$A = \pi r^2$$

$$= \frac{\pi}{4} \cancel{\rho}^2$$

$$dA = \frac{\pi}{4} (2 \cancel{\rho} d\rho)$$

$$\frac{dA}{A} = \frac{\cancel{\pi}}{4} (2 \cancel{\rho} d\rho)$$

$$\frac{\cancel{\pi}}{4} \cancel{\rho}^2$$

$$= \frac{2 d\rho}{\cancel{\rho}}$$

$$\frac{d\rho}{\cancel{\rho}} = \frac{dL}{L} (-\gamma)$$

$$= -\gamma \frac{dL}{L}$$

$$\therefore \frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \left( -2\gamma \frac{dL}{L} \right)$$


$$= \frac{d\rho}{\rho} + (1+2\gamma) \frac{dL}{L}$$

$$= \frac{d\rho}{\rho} + (1+2\gamma) S \quad \therefore S = \frac{dL}{L}$$

$$= \left( \frac{d\rho}{\rho} \frac{1}{S} + 1 + 2\gamma \right) S \quad (\text{shown})$$

4)

$$R_1 = R_2 = R_3 = 120 \Omega$$

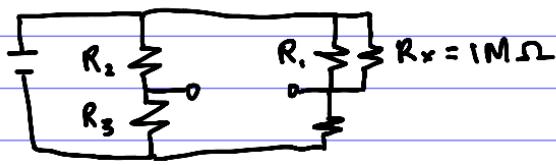

$$\frac{dR_g}{R_g} = G^* s$$

$$\frac{dR_i}{R_i} = \frac{R_i / R_x}{R_i} - \frac{R_i}{R_i}$$

$$= \frac{R_x}{R_i + R_x} - 1$$

$$= \frac{R_x}{R_i + R_x} - \frac{R_i + R_x}{R_i - R_x}$$

$$= -\frac{R_i}{R_i + R_x}$$

$$\approx -\frac{R_i}{R_x} \quad \because R_i \ll R_x$$

$$= -\frac{120}{1 \times 10^6}$$

$$= -1.2 \times 10^{-4}$$

$$\frac{dR_g}{R_g} + \frac{dR_i}{R_i} = 0$$

$$\frac{dR_g}{R_g} = -\frac{dR_i}{R_i}$$

$$= -(-1.2 \times 10^{-4})$$

$$= 1.2 \times 10^{-4}$$

$$G^* s = 1.2 \times 10^{-4}$$

$$G^* (100 \times 10^{-6}) = 1.2 \times 10^{-4}$$

$$G^* = 1.2$$

4) Why is  $G^* = 1.2$ , which is much less than the expected value of 2.1?

1. Poor bonding.
2. Possible misalignment
3. Long wire resistance



$$SG = \frac{dR_0}{R_0}$$

$$SG^* = \frac{dR_0}{R_g}$$

$$R_g = 2r_0 + R_0$$

$$SG^* = \frac{d(2r_0 + R_0)}{2r_0 + R_0}$$

$$= \frac{dR_0}{2r_0 + R_0}$$

$$= \frac{dR_0}{R_0} \left( \frac{R_0}{2r_0 + R_0} \right)$$

$$= SG \left( \frac{R_0}{2r_0 + R_0} \right)$$