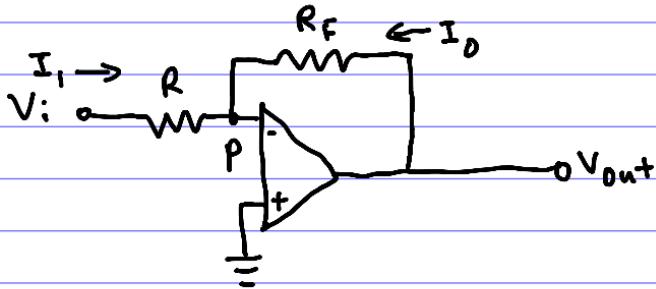


1) Op-amp with infinite input resistance and zero output resistance:  $I_o = -I_i$ ,



$S_0$ ,

$$\frac{V_p - V_o}{R_f} = - \frac{V_p - V_i}{R}$$

$$R(V_p - V_o) = -R_f(V_p - V_i)$$

$$V_p(R_f + R) = RV_o - V_i R_f.$$

Finite loop gain,  $A = -\frac{V_o}{V_p}$ ,

$$V_p = -\frac{V_o}{A}$$

$$\therefore -\frac{V_o}{A}(R_f + R) = RV_o - V_i R_f$$

$$-V_o(R_f + R + AR) = V_i AR_f$$

By definition, op-amp gain,  $G = \frac{V_o}{V_i}$ :

$$-V_o(R_f + R + AR) = V_i AR_f$$


$$\frac{V_o}{V_i} = \frac{-AR_f}{R_f + R + AR}$$

$$G = \frac{-AR_f}{R_f + R + AR} \text{ (shown)}$$

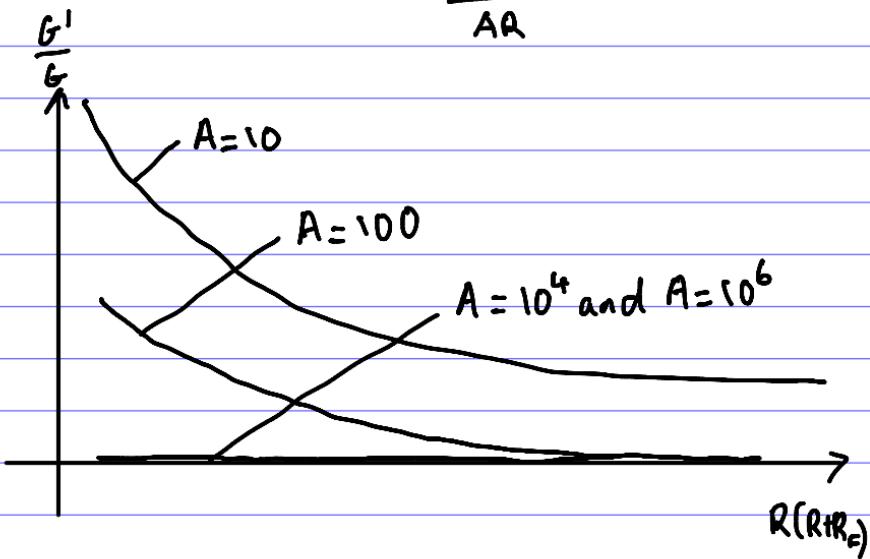1) For large open loop gain  $A$ ,  $AR \gg (R+R_F)$ ,

$$G' = -\frac{R_F}{R}$$

$$\begin{aligned}\frac{G'}{G} &= \frac{R_F}{R} \times \frac{R_F + R + AR}{AR} \\ &= \frac{R_F + R + AR}{AR} \\ &= 1 + \frac{R + R_F}{AR}\end{aligned}$$



A practical op-amp has very high input impedance ( $Z_i > 10^7 \Omega$ ), low output impedance ( $Z_o < 100 \Omega$ ), and high open-loop gain ( $A$  about  $10^5 - 10^6$ ), and the values of  $R$  and  $R_F$  are typically in the  $k\Omega$  to the  $M\Omega$  range, so it is valid to use the second equation.

$$2a) \quad G = 1 + \frac{R_F}{R}$$

$$V_P = \left( 1 + \frac{R_2}{R_1} \right) V_i$$

$$= \left( 1 + \frac{6}{1} \right) (1)$$

$$= 7V$$

$$V_o = \left( 1 + \frac{R_4}{R_3} \right) V_P$$

$$= \left( 1 + \frac{1}{1} \right) (7)$$

$$= 14V$$

$$b) \quad V_P = - \left( \frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2 \right)$$

$$= - \left( \frac{10}{1} (0.1) + \frac{10}{10} (1) \right)$$

$$= -2V$$

$$V_o = - \left( \frac{R_6}{R_4} V_P + \frac{R_6}{R_5} V_3 \right)$$

$$= - \left( \frac{10}{1} (-2) + \frac{10}{1} (1) \right)$$

$$= 10V$$

3) Since signals above 2.5kHz are not wanted, a low pass filter is needed. The cut-off frequency must be at least 2.5kHz and less than about 3kHz where the accelerometer response becomes more than 1.

$$f_c = \frac{1}{2\pi RC}$$

$$RC = \frac{1}{2\pi f_c}$$

$$RC = \frac{1}{2\pi(2500)}$$

$$\begin{aligned} &= 6.366197724 \times 10^{-5} \\ &\approx 6.37 \times 10^{-5} \end{aligned}$$

$\therefore$  Let  $R = 63.7 \Omega$ ,  $C = 1 \text{ nF}$


$\frac{1}{f_c}$  is a good approximation of the time constant.

$$\therefore T \approx \frac{1}{f_c}$$

3) The frequency response of a filter is:

$$\begin{aligned}M(f) &= \frac{1}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}} \\&= \frac{1}{\sqrt{1 + \left(\frac{2500}{2500}\right)^2}} \\&= \frac{1}{\sqrt{2}}\end{aligned}$$

$$\approx 0.707$$

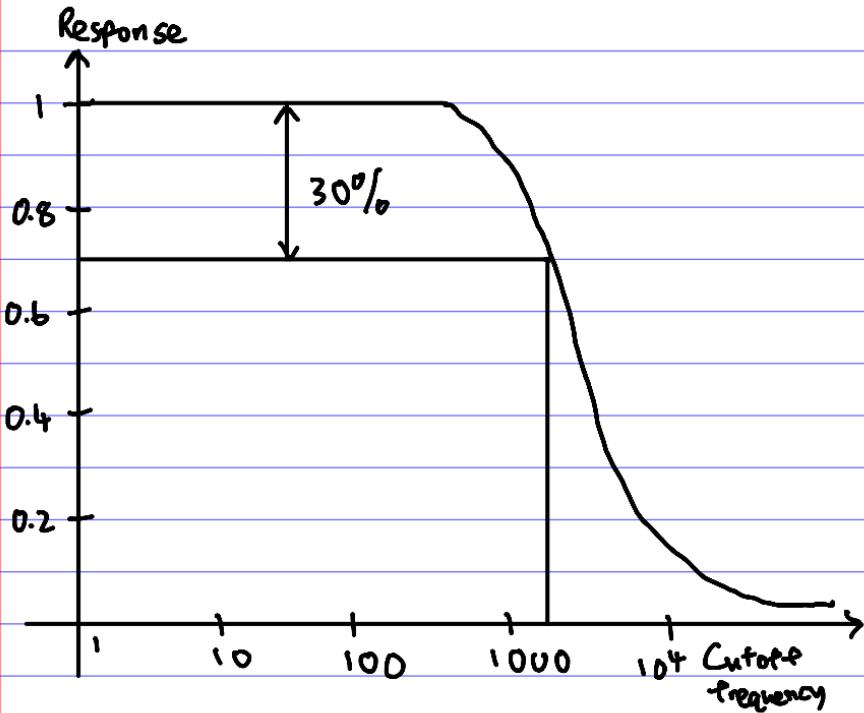

### 3) Frequency Response Curve

Amplitude Ratio ( $A_{out}/A_{in}$ )

